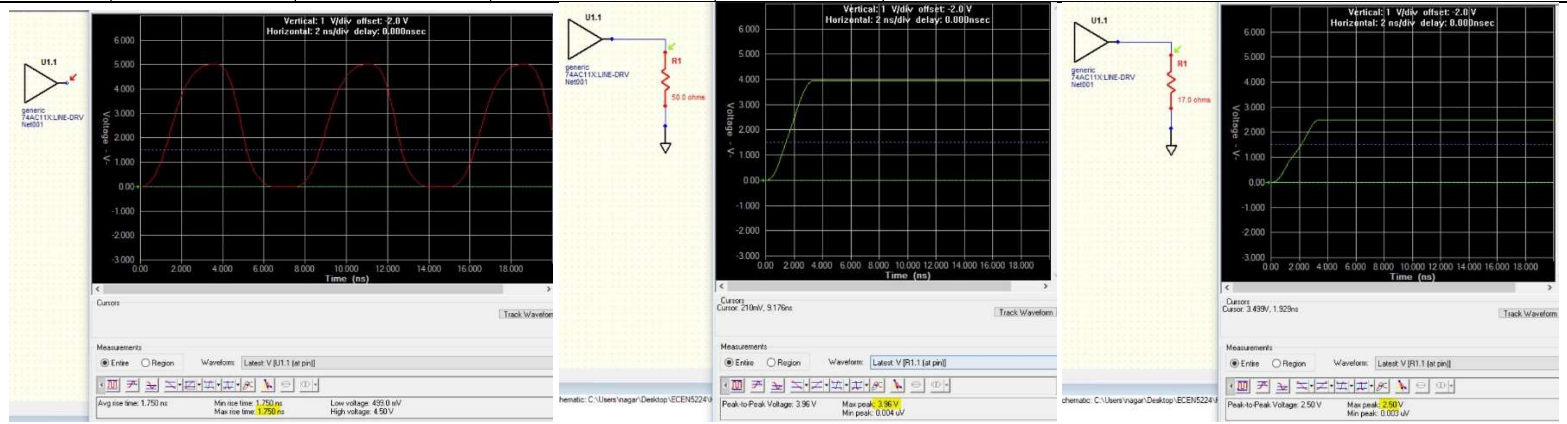
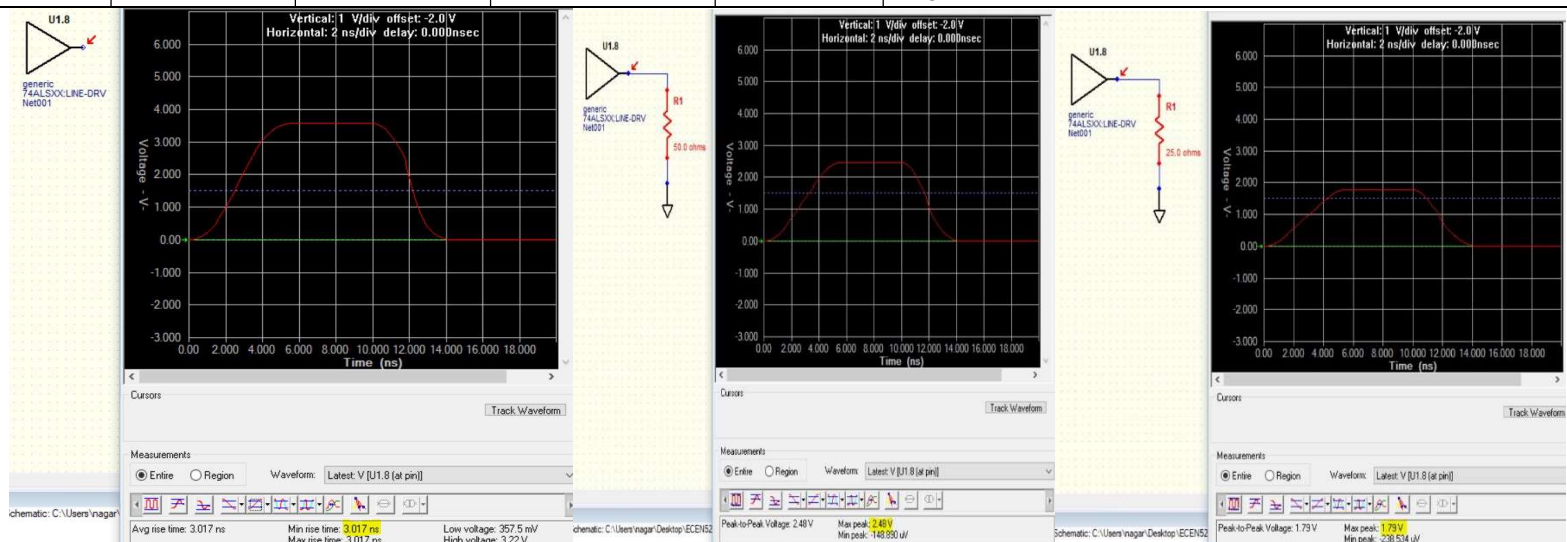


Goal: The goal of this lab is to get a hands-on experience to characterize Drivers based on Rise and fall times, Source Impedance, Open circuit voltage and apply all the major termination strategies and tabulate their respective advantages and disadvantages. Also, tabulate the power dissipation. Tool used is Hyperlynx.


Plan: The plan is to theoretically anticipate the source impedance and to theoretically apply the termination strategies to Transmission and predict the best approach considering the power, extra components and so on. The same needs to be verified in Hyperlynx.


Characterize two driver models: 74ACT11, TDR, IDT 74FCT

Driver	Rise Time (ns) (10%-90%)	Fall Time(ns) (10%-90%)	Source Impedance (ohm)	Open Circuit Voltage (V)	Comments
74ACT11	1.75	1.347	17	5	The fall time < rise time as expected since Rise Time is governed by PMOSFET whose switching time is comparatively higher than NMOSFET which governs the fall time. As per simulation, for a termination of 50 ohm at the driver, the voltage across resistor is 3.96V. So, applying Voltage Divider equation, $3.96 = 5 * 50 / (R_s + 50)$. R_s turns out to be 17 ohm. When the 50 ohm termination is replaced with 17 ohm, the voltage across resistor is 2.5V.
					
74ALSXX	3.017	2.074	25	3.58	The fall time < rise time as expected since Rise Time is governed by PMOSFET whose switching time is comparatively higher than NMOSFET which governs the fall time. As per simulation, for a termination of 50 ohm at the driver, the voltage across resistor is 2.48V. So, applying Voltage Divider equation, $2.48 = 3.58 * 50 / (R_s + 50)$. R_s turns out to be 25 ohm. When the 50 ohm termination is replaced with 25 ohm, the voltage across resistor is 1.79V.
					

Pick one of the drivers: Build a transmission line circuit. How long can it be without termination?

Driver	Maximum Transmission Line length without termination (in)	Comments
74ACT11	3.2	The Receiver is a TDR model. For Transmission Line length in inch lesser than rise time in ns, there should absolutely no distortion in the received signal as per the thumb rule. For length greater than 3 inch, the Monotonicity at the logic low level will be affected with further increase of trace length due to excess ringing. However, the logic low level goes till -0.8V and is neglected. The rise time being 1.74 ns, the quality of the signal when it travels a length of 1.74 inch cannot be guaranteed as it heavily depends on the Receiver input characteristics like Gate capacitance.

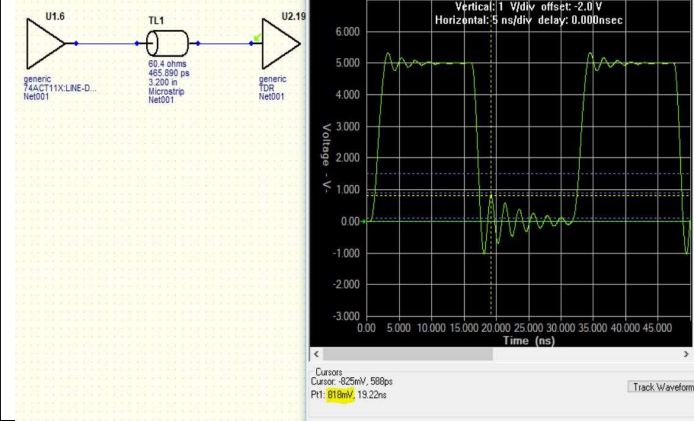


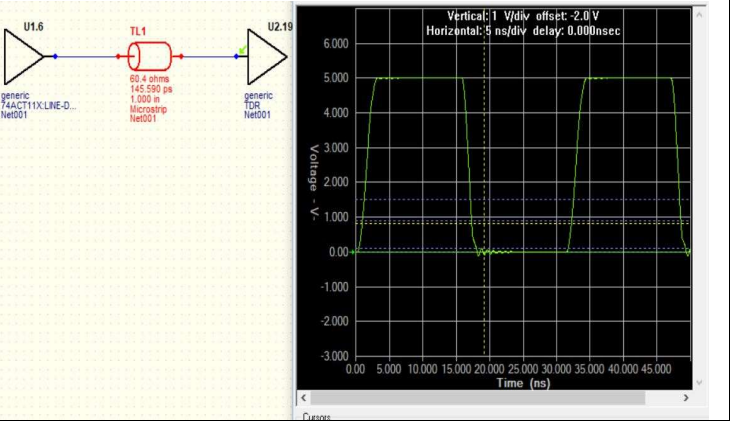


Engineer the five different termination schemes and optimize each one. Do some have advantages?



Note: The transmission line considered is a simple, 50-ohm, 5 ns delay type. The Receiver is a TDR model.

Termination Type	Resistor added (ohm)	Vlow (V)	Vhi (V)	Acceptable ?	Comments
Source Series	33	-0.639	5	Yes	<p>The Driver source resistance being 17 ohm, if a series resistor of 33 ohm is added near to driver in series to equate to transmission line impedance of 50 ohm, the signal sees a uniform impedance of 50 ohm throughout. Although the Logic high level is more than 5V and logic low level is less than 0, they are acceptable. Without the series resistor, there are very high ringing due to impedance mismatch. The same is observed in the below simulation.</p> <p>Advantages:</p> <ul style="list-style-type: none">1. Low power dissipation compared to other terminations2. Easy to implement since only a single component required and occupies low area on PCB <p>Disadvantages:</p> <ul style="list-style-type: none">1. Larger values might increase the rise time at the RX gate capacitance and the current thereby increasing the impedance

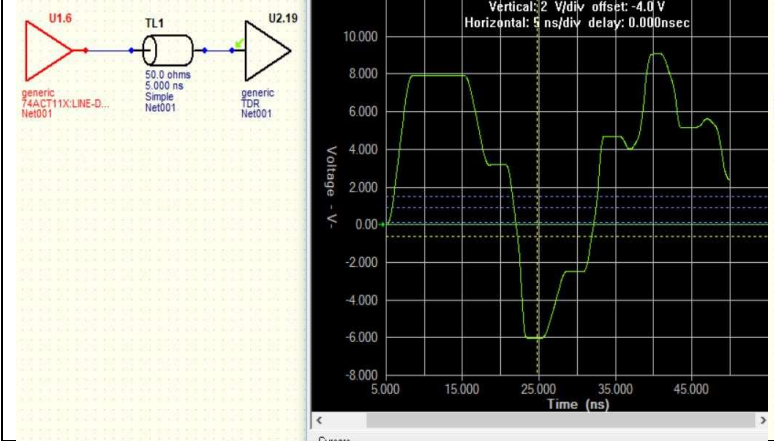

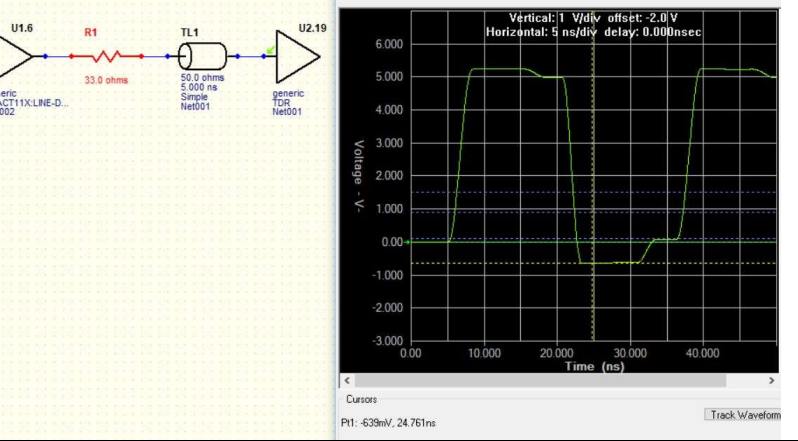

Far End Shunt to Vss	33	-0.639	4	Yes	The Driver source resistance being 17 ohm, if a shunt resistor of 68.4 ohm is added near to RX to equate to transmission line impedance of 50 ohm, the signal sees a uniform impedance of 8.4 ohm throughout. Although the Logic logic low level is less than 0, its are acceptable. Without the shunt resistor, there are very high ringing due to impedance mismatch. The same is observed in the below simulation.
-----------------------------	----	--------	---	-----	---

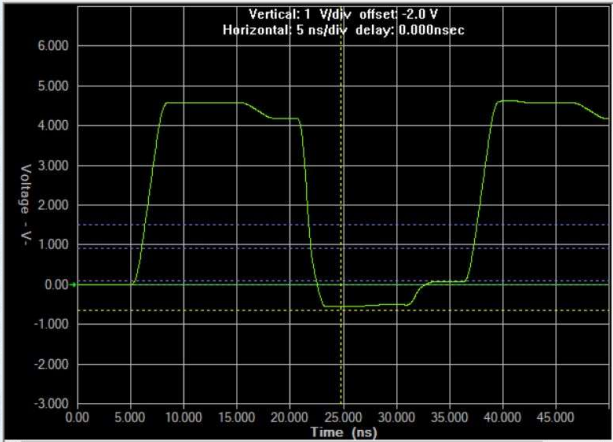 


Advantages:

1. Easy to implement since only a single component required and occupies low area on PCB

Disadvantages:

1. Very high Steady state power dissipation

Far End RC	68.4 ; C= 100 nF	-0.639	4	Yes	
-------------------	------------------	--------	---	-----	--

 



Advantages:

1. power dissipation is negligible due to capacitance

Disadvantages:

1. This is suitable only for signals with a rock solid 50% duty cycle due to capacitance as anything other than that would have disproportionate Rise and fall times leading to ISI
2. Comparatively occupies more area compared to other terminations

Far End Thevenin	R1=100; R2=100	0.2	4.5	Yes	The far end Thevenin network should be such be such that the Vcc should be equal to the signal voltage from the driver and the equivalent parallel value of the resistors be equal to Z0 of transmission line. This ensures proper termination as there would be uniform impedance throughout the path. The same is observed in the below simulation.
-------------------------	----------------	-----	-----	-----	---

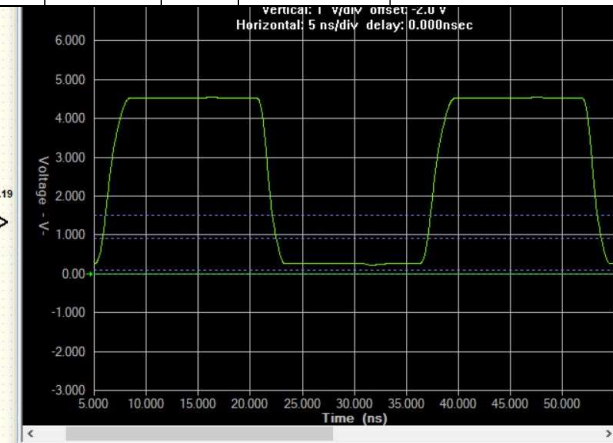 

Disadvantages:

1. This needs an additional regulator to supply voltage equal to the open circuit voltage of the driver signal
2. There has to be minimum impedance between Voltage and RTN ; otherwise it may lead to Ground bounce and other errors.
3. Comparatively occupies more area compared to other terminations

Far End Shunt to Vtt	50	0.4	4.5	Yes	The Driver source resistance being 17 ohm, if a shunt resistor of 68.4 ohm is added near to RX to equate to transmission line impedance of 50 ohm, the signal sees a uniform impedance of 8.4 ohm throughout. Although the Logic logic low level is less than 0, its are acceptable. Without the shunt resistor, there are very high ringing due to impedance mismatch. The same is observed in the below simulation.
<div style="display: flex; justify-content: space-between;"> <div style="width: 25%;"> </div> <div style="width: 45%;"> </div> <div style="width: 30%;"> <p>Advantages:</p> <ol style="list-style-type: none"> 1. Low power dissipation compared to other terminations 2. Easy to implement since only a single Resistor required and occupies low area on PCB <p>Disadvantages:</p> <ol style="list-style-type: none"> 1. This needs an additional regulator to supply voltage of half of the open circuit voltage of the driver signal 2. There has to be minimum impedance between Voltage and RTN ; otherwise it may lead to Ground bounce and other errors. </div> </div>					

Calculate the average power dissipation in each approach, assuming driver output resistance is 0.

Termination Type	Power Dissipation Formula	Power Dissipation (W)	Comment
Source Series	$0.5 \cdot (0)/50$	0	The Voltage across the Resistor is negligible as the other end is a very high impedance (RX)
Far End Shunt Vss	$0.5 \cdot (5^2)/50$	0.25	50% duty cycle considered for the signal
Far End RC	$0.5 \cdot (0.5 \cdot 5)^2/50 + 0.5 \cdot (0.5 \cdot 5)^2/50$	0.125	
Far End Thevenin	$0.5 \cdot (5^2)/100 + 0.5 \cdot (5^2)/100$	0.25	
Far End Shunt to Vtt	$0.5 \cdot (0.5 \cdot 5)^2/50 + 0.5 \cdot (0.5 \cdot 5)^2/50$	0.125	

Conclusions / Lessons Learnt:

1. Analyze the characteristics of a Driver pin before using it on board
2. Make sure Length (in) < Rise time (ns) for any signal to avoid signal distortion. If this condition cannot be met due to board dimensions, use any major termination strategy.
3. Source Series termination is the best approach but too much of a source series resistor might increase the rise time at Receiver
4. Avoid Far End Thevenin Termination as it needs many additional components and has high power dissipation. Also, the impedance between the Voltage and Return must be minimum to avoid any Ground bounce or related issues
5. Use Far End RC termination only when the signal duty cycle is 50%. Else it may lead to ISI